
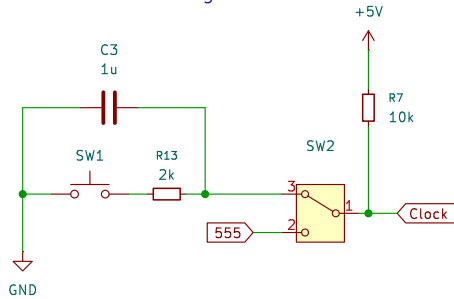



### Tipkalo i ulaz radnog takta

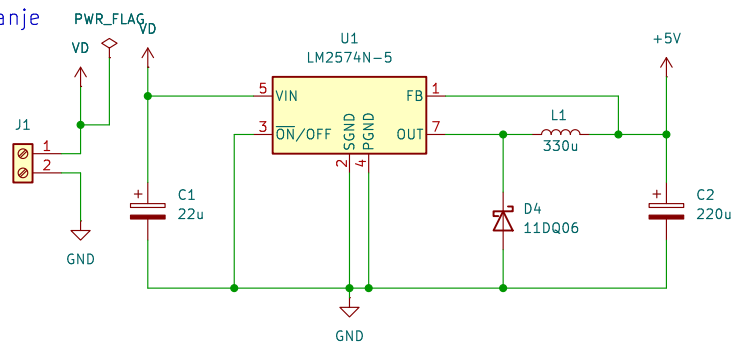


### Napajanje




### LED diode

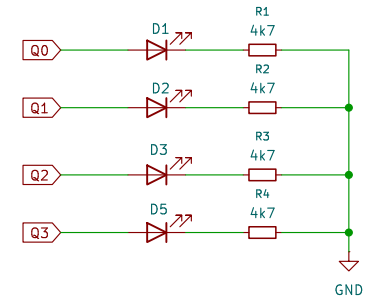


### 555 Timer

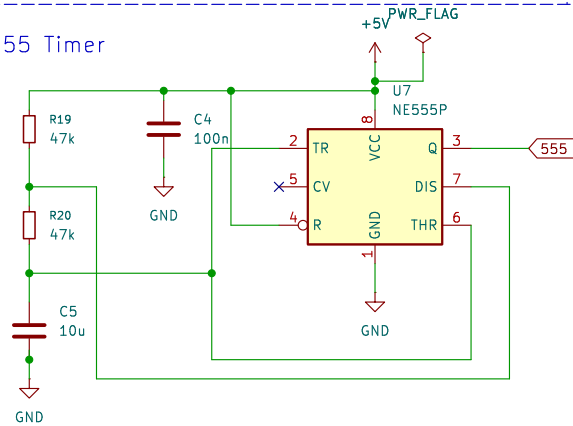


### Reset brojača

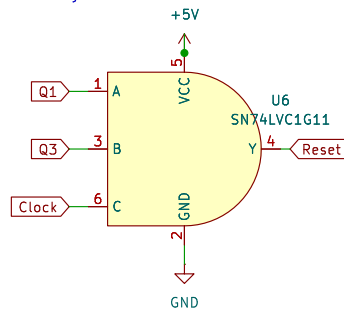

### JK bistabil

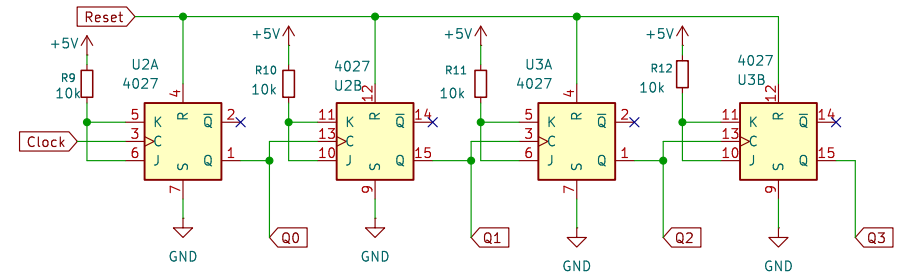


### Napajanje bistabila

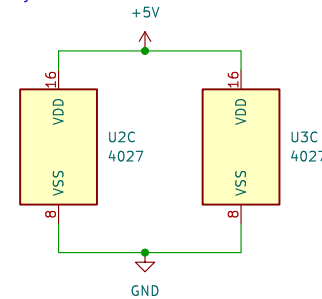
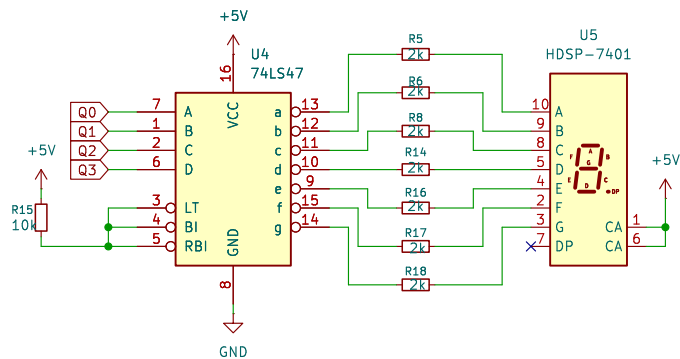
### Montažne rupe

- H1 MountingHole
- H2 MountingHole
- H3 MountingHole
- H4 MountingHole



Izradio: Gabriel Šolčić  
TVZ – Tehničko veleučilište Zagreb

Sheet: /  
File: PTP\_project1.kicad\_sch

**Title: BCD brojač**

Size: A4 Date: 2025-10-21

KiCad E.D.A. 9.0.3

Rev: 0

Id: 1/1